

Final Design

Battery Powered Analog Section

1. Design battery boost circuit 3.6v to 5 and 5 to -5v,
 - Add connector for input;
 - Add circuit protections;
 - Add test point of all voltages
2. Design 0.5 A battery charger circuit
3. Design ECG Analog front end;
 - Add test point of analog front end output
 - you can use LMC7660 insted of LM2776 and INA188 instead of AD620
4. add battery input connector and 5v input connector for battery charger

DC High Power Section

- 1.Design 12v to 5v buck convertor ,5v to 3.3v linear regulator
 - Add connector for 12v input;
 - Add circuit protections;(reverse polarity with p channel mosfet)
 - Add test point of all voltages
2. Design 12 v 0.5A Dc motor driver(add motor connector)
3. Design 12 v 1A Relay circuit(add connector for relay)
4. Design 12v 1A led driver(add connector for led)

Add test point or header to control dc motor, relay circuit and led driver

*Design 4 layer Pcb(signal-gnd-power-signal)